
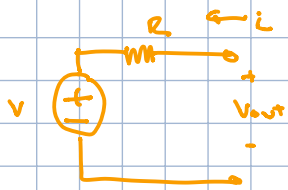


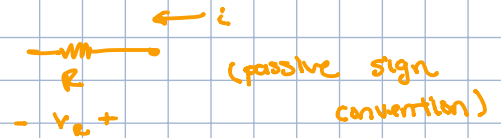
Thevenin Equiv is used to simplify a complex circuit into a voltage source and a resistor  $R$



$$V_{out} = Ri + V$$



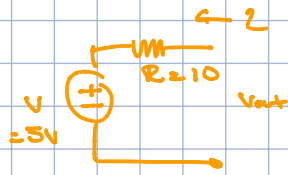So given a circuit, let's set a hypothetical current value through circuit.




equiv R

$$V_o = 10i + 5$$

different  $i$  values changes voltage output.  
current

ex.

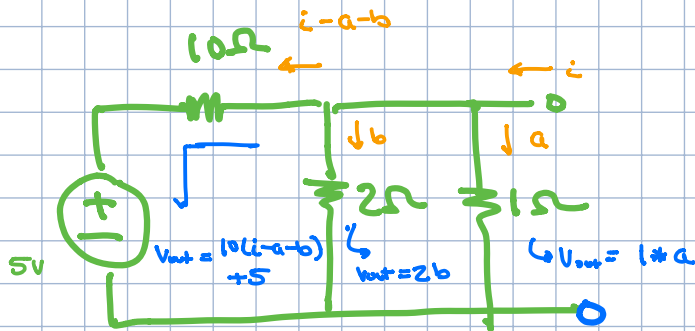

$$V = 1a = 2b = 10(i - a - b) + 5$$

(let's take this equation)

$$\frac{V}{1} = a \quad \frac{V}{2} = b$$

$$V = 10 \left( i - \frac{V}{1} - \frac{V}{2} \right) + 5$$

$$V = 10i - 10V - 5V + 5$$


$$V = 10i - 15V + 5$$

$$16V = 10i + 5$$

$$V = \frac{10}{16}i + 5/16$$

equiv R

ex.

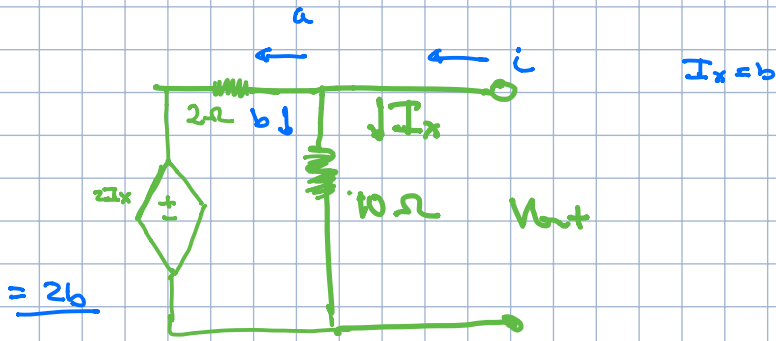

$$V_{out} = 2b + 2a \quad \text{and} \quad V_{out} = 10b \quad \text{and} \quad a + b = i$$

$$V_{out} = \frac{2V_{out}}{10} + 2a$$

$$V_{out} = \frac{V_{out}}{5} + 2 \left[ i - \frac{V_{out}}{10} \right]$$

$$V_{out} = \frac{V_{out}}{5} + 2i - \frac{V_{out}}{5}$$

$b = V_{out}/10$   
 $a = i - b$   
 $a = i - \frac{V_{out}}{10}$

$$V_{out} = 2i$$

$$R_{eq} = 2$$

$$V_{eq} = 0V$$