

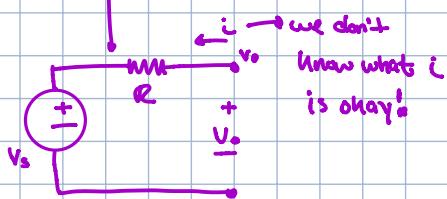
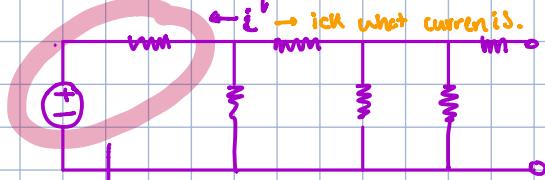


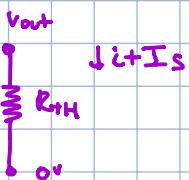Thevenin Equivalence and Norton → SOURCE TRANSFORMATION.



$$v_o = v_s + i \cdot R_{TH}$$

↳ voltage when current changes.

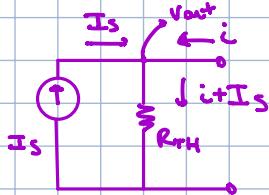

$$\begin{aligned} v_o &= R_{TH} \cdot (i + I_s) \\ &= R_{TH} \cdot i + R_{TH} \cdot I_s \end{aligned}$$




$$v_o = i \cdot (R_{TH}) + v_s$$

$$v_o = i \cdot (R_{TH}) + R_{TH} \cdot I_s$$

$$\therefore v_s = R_{TH} \cdot I_s$$

Thevenin and Norton

1.

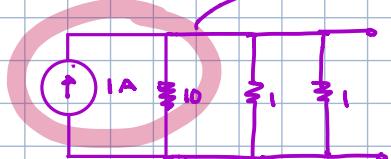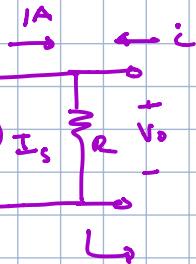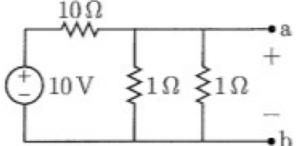


$$\frac{1}{10} + \frac{10}{10} + \frac{10}{10} = \frac{1}{R}$$

$$R_{TH} = \frac{10}{21} \Omega$$



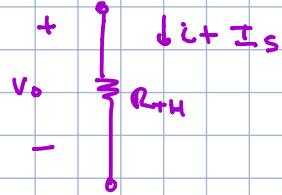Norton current = I_s
 $R_{TH} = 10/21 \Omega$





$$V_o = R_{TH} (i + I_s)$$

$$V_o = R_{TH} i + R_{TH} * I_s$$

i test


2.

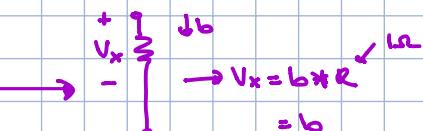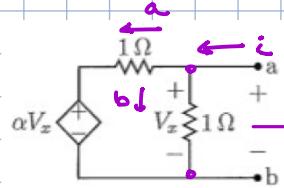

(Hint: answer is in terms of α)

boi, that's not really a hint

$$i = a + b$$

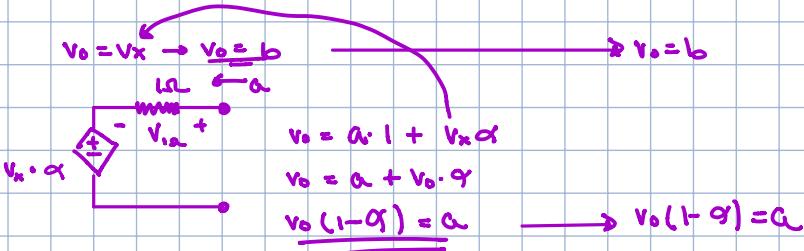

$$i = a + b$$

$$i = V_o(1 - \alpha) + V_o$$



$$i = V_o(1 - \alpha + 1)$$

$$i = V_o(2 - \alpha)$$

$$V_o = \frac{i}{(2 - \alpha)}$$

$$R_{TH} = \frac{1}{2 - \alpha}$$

3.

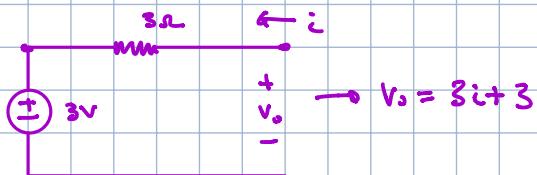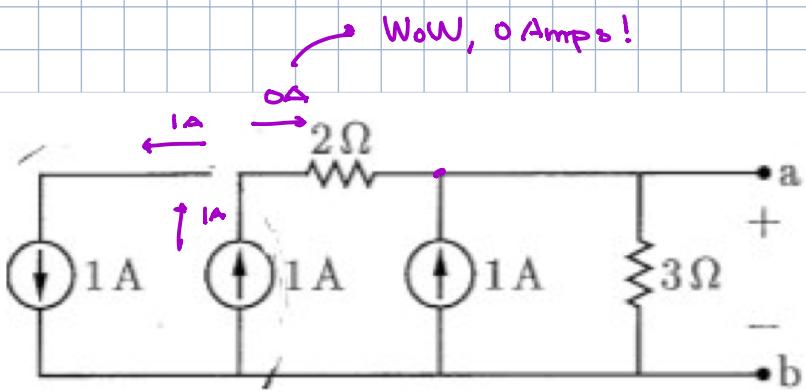

4. * I call this move the **Patrick Mahomes**, because

You DON'T HAVE TO LOOK AT THE

CIRCUIT TO GET THE


Sorry, I thought
this would make
you laugh. Continue
studying.

RIGHT ANSWER HAHAHA

$$v = 10V \quad i_L = 0A$$

$$v = -10V \quad i_L = 2A$$

reference
the circuit
as thevenin
equiv.

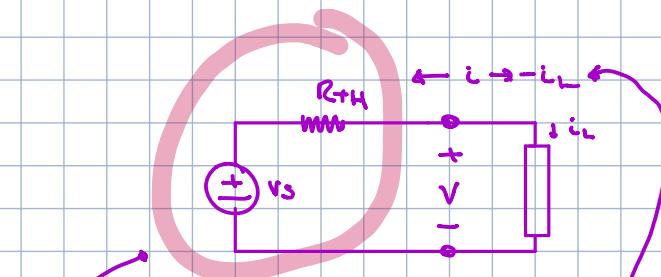

$$V = R_{TH} * i + V_s$$

$$10 = R_{TH} + (-3) + 3 \rightarrow 10 = V_s$$

$$-10 = R_{TH} * (-2) + 3 \leftarrow$$



$$-10 = R_{TH} * (-2) + 10$$

$$-20 = R_{TH} * (-2)$$

$$R_{TH} = -20 / -2 = 10 \Omega$$

$$R_{TH} = 10 \Omega$$

5.

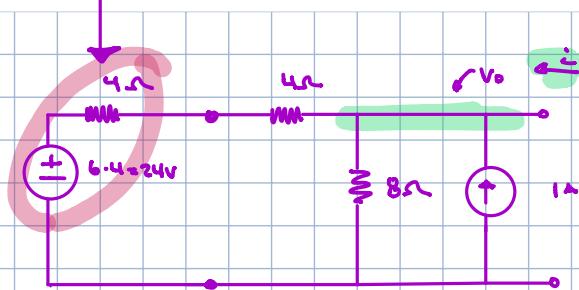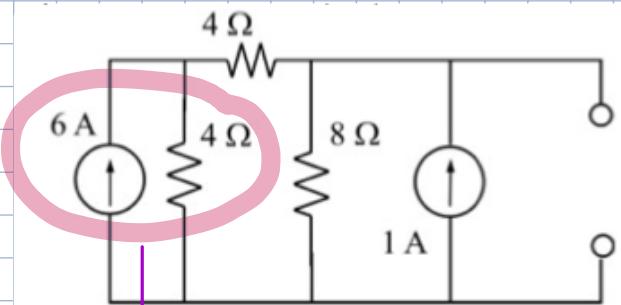

This is interesting
* okay, to be honest, I'm way too lazy to continue, so I'm going to do much day.

→ Also, the goal is to finish ASAP so...

↳ if you want to learn more, or just use source, come to office hours.

$$\left(\frac{24 - V_o}{4+4} + \frac{0 - V_o}{8} + 1 + i_L = 0 \right) 8$$

$$24 - V_o - V_o + 8 + 8i_L = 0$$

$$-2V_o + 32 + 8i_L = 0$$


$$(32 + 8i_L = 2V_o) \frac{1}{2}$$

$$16 + 4i_L = V_o$$


$$\boxed{V_s = 16V} \quad \boxed{R_{TH} = 4\Omega}$$

$$i_a = 16/4 = 4A$$

6.

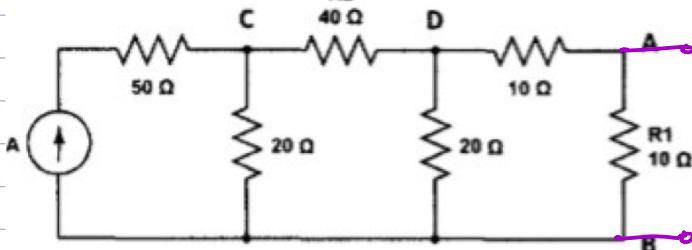
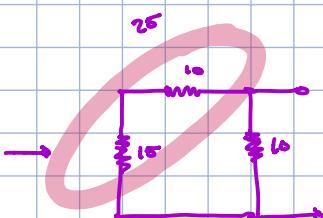
$$\frac{40 \cdot 20}{20 + 60} = \frac{1200}{80} = \frac{30}{2} = 15$$




$$\frac{15}{25} = \frac{3}{5} \rightarrow \text{OKAY, STOP}$$

$$\therefore R_{TH} = 25\Omega$$


THIS IS THE LOAD

7.

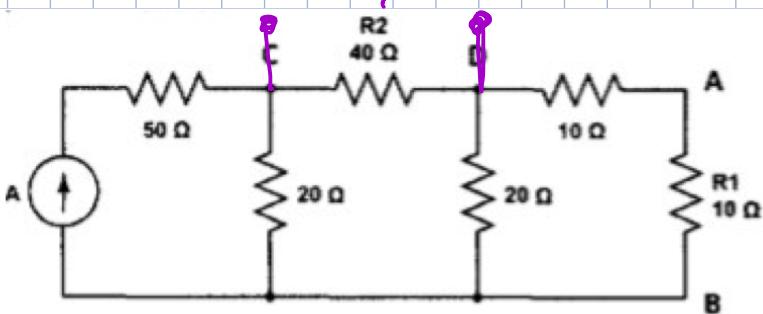


not going to make the same mistake again.

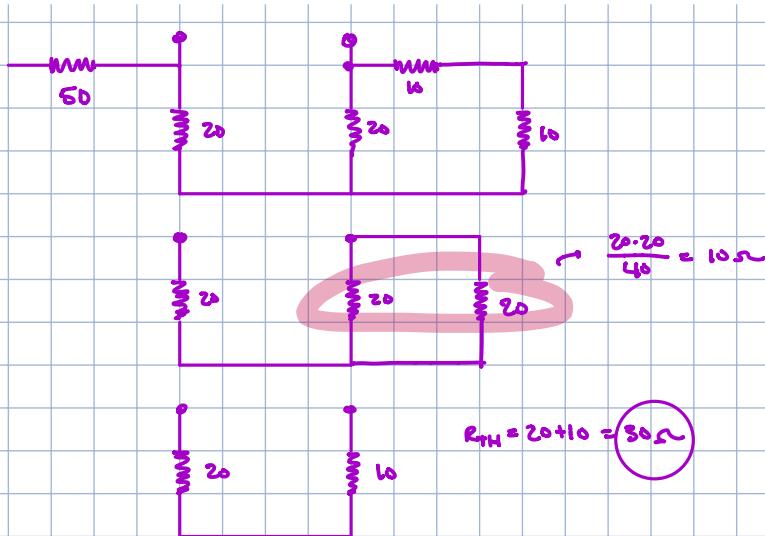
I'm going to take it out because it is R_{load} .





8.

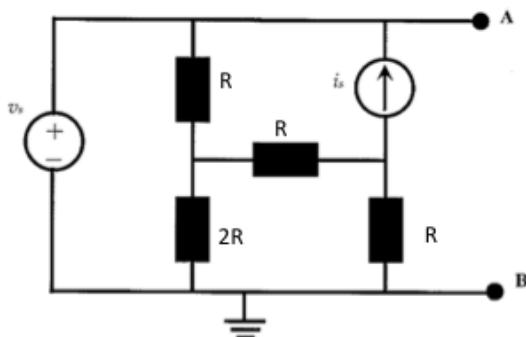



Wow
short circuit

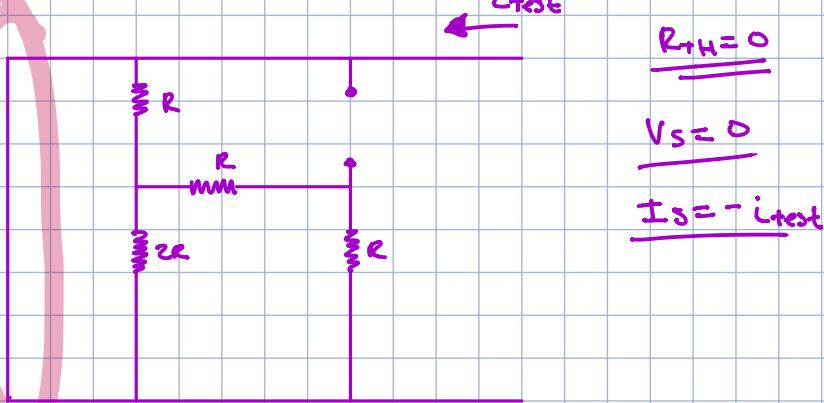


9.

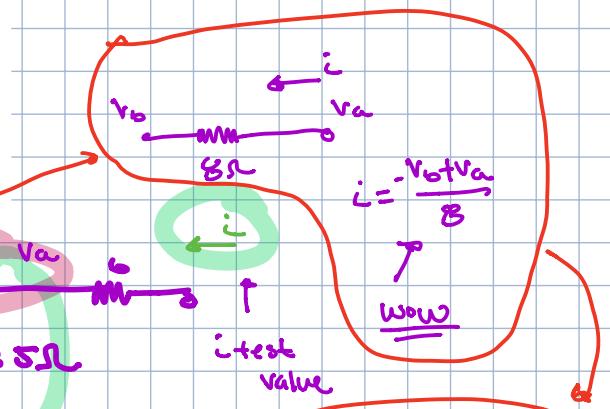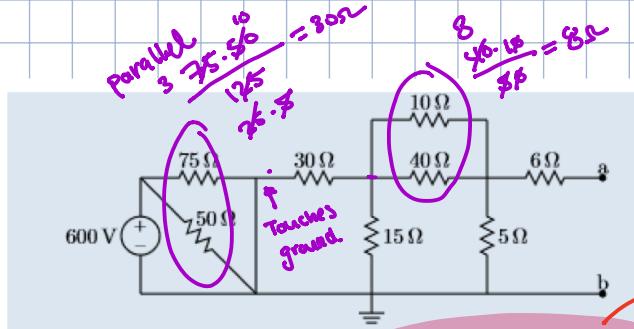

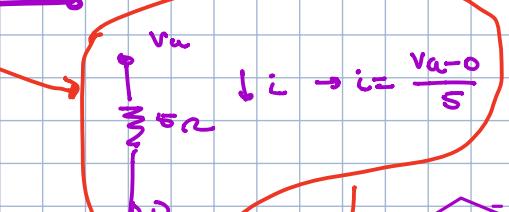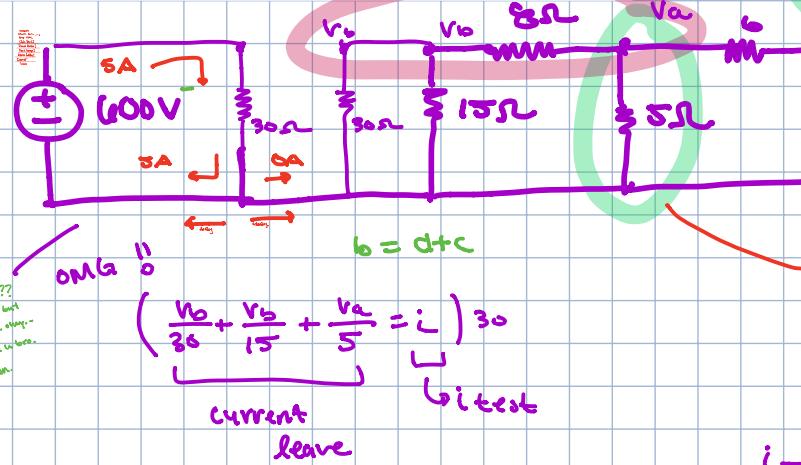Hey LTCA
 - Do Super nodes??
 - I need anything last
 - source more
 - or if I get it wrong,
 - Thanks man


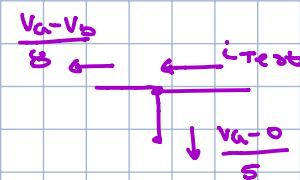
$$i_T = \frac{-V_o + V_a}{B} + \frac{V_a - 0}{5}$$



$$\begin{aligned} V_b + 2V_b + 6V_a &= 30i \\ i &= \frac{-V_b + V_a}{B} + \frac{V_a}{5} \end{aligned}$$

$$\frac{3V_b + 6V_a = 30i}{3}$$

$$\begin{aligned} 40i &= -5V_b + 5V_a + 8V_a \\ 40i &= -5V_b + 13V_a \end{aligned}$$


($V_b + 2V_a = 10i$) (+5)

Two equations

$$\begin{aligned} 5V_b + 10V_a &= 50i \\ -5V_b + 13V_a &= 40i \end{aligned}$$

$$23V_a = 90i$$

$$V_a = \frac{90}{23}i$$

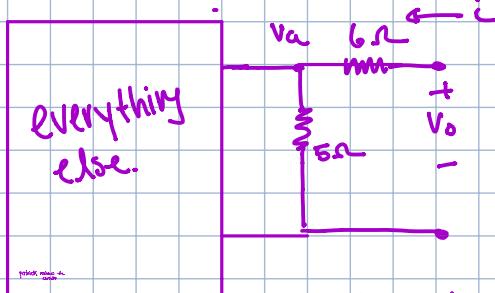

$$V_o = 6i + V_a$$

$$V_o = 6i + \frac{90}{23}i$$

$$V_o = 9.913i$$

$$\therefore R_{TH} = 9.913$$

if you understand
this, then u
are super ready.
if not, then look
below.

Was that quick?
Bro, No, I can go quicker..

